


How Computers Work

Lecture 4

Computer Arithmetic

How Computers Work Lecture 4 Page 1

A Descending Data Flow View of the Beta

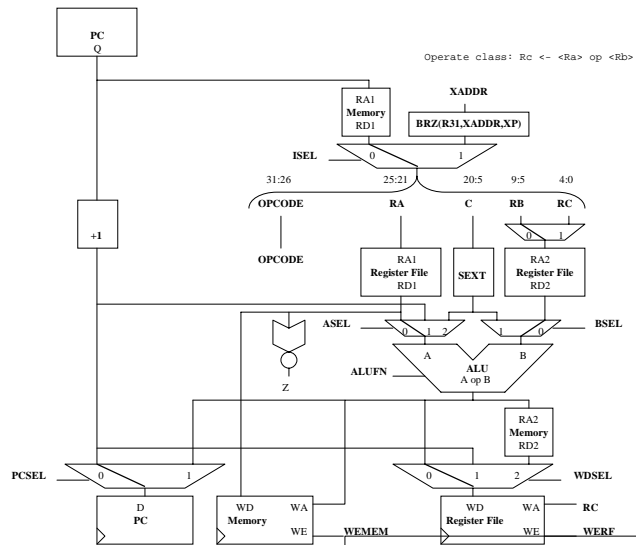


How Computers Work Lecture 4 Page 2

What are we going to learn today?

- How to build the *Arithmetic/Logical Unit*
 - Integer adder and multiplier architectures
 - Time/Space/Cost Trade-offs

How Computers Work Lecture 4 Page 3


The 74181 ALU

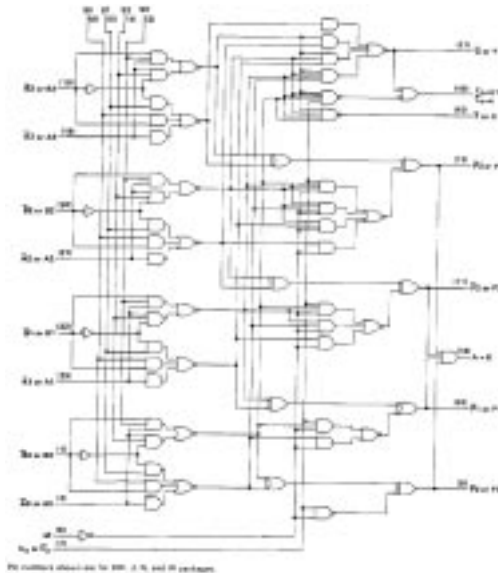

How Computers Work Lecture 4 Page 4

A Wild and Crazy Idea:

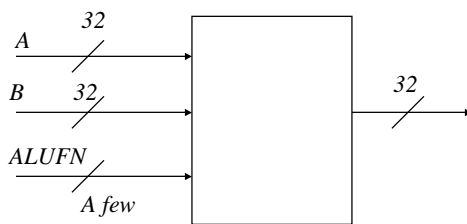- Arithmetic / Logic Unit is describable by a table:
 - ergo, we can implement it with a memory:




Bad Idea, because:
 2^{70} is a large number of rows!

How Computers Work Lecture 4 Page 5

A 1 Bit Full Adder


C_i	A	B	S	C_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

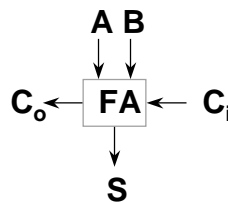- Generates 1 sum bit, carry
- Can be cascaded to N bits



How Computers Work Lecture 4 Page 6

Ripple-carry N-bit adder:

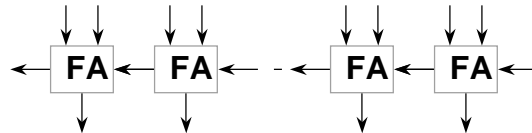

Problem: It's *Slow!*

How Computers Work Lecture 4 Page 7

What is C_o as a function of C_i , A , B ?

C_i	A	B	S	C_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$C_o = \overline{C_i}AB + C_i\overline{A}B + C_iA\overline{B} + C_iAB$$

How Computers Work Lecture 4 Page 8

But What is Co really ?

C_i	A	B	S	C_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$C_o = 1$ if 2 or more inputs are 1 !

How Computers Work Lecture 4 Page 9

How can we build simplified logic?

Example: Full Adder : K-Map

C_i	A	B	S	C_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

		A			
		0	1	0	1
S:	—				
	C_i	1	0	1	0
		B			
		A			
		0	0	1	0
C_o :	—				
	C_i	0	1	1	1
		B			

How Computers Work Lecture 4 Page 10


The Karnaugh Map

Characteristics:

- 1: Unit-Distance Input Labels
- 2: Wrap-Around

How Computers Work Lecture 4 Page 11


AND

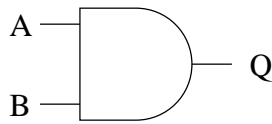

		Q
—	0	—
A	0	—
—	1	—
—	0	B

How Computers Work Lecture 4 Page 12


OR

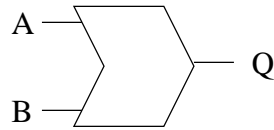

Q	
A	0
A	1
B	1
B	1

How Computers Work Lecture 4 Page 13

XOR

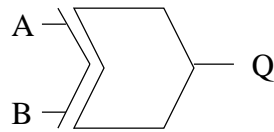

Q	
A	0
A	1
B	0
B	1

How Computers Work Lecture 4 Page 14

Q: What is Cout?

		A				
		0	0	1	0	
$\overline{C_i}$		0	1	1	1	
		B				

$$C_o = \overline{C_i}AB + C_i\overline{A}B + C_iA\overline{B} + C_iAB$$

How Computers Work Lecture 4 Page 15

Q: What is Cout?

		A				
		0	0	1	0	
$\overline{C_i}$		0	1	1	1	
		B				

A: (A and Ci) or (A and B) or (B and Ci)

A: (A Ci) + (A B) + (B Ci)

A: A Ci + A B + B Ci

How Computers Work Lecture 4 Page 16


How about S ?

C_i	A	B	S
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

	A			
	0	1	0	1
C_i	1	0	1	0
	B			


How Computers Work Lecture 4 Page 17

Parity

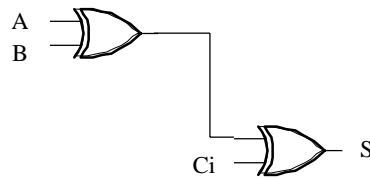

How Computers Work Lecture 4 Page 18

Tree Structure

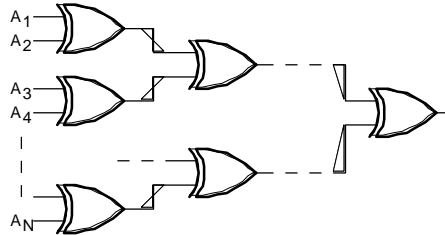

N-input TREE has $O(\log(n))$ levels...


Signal propagation takes $O(\log(n))$ gate delays.

$O(n)$ gates.

How Computers Work Lecture 4 Page 19

An Idea !

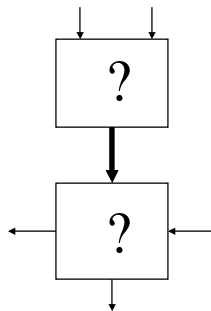- Speed things up by doing as much work as possible on A & B Inputs **before** the carry arrives:



How Computers Work Lecture 4 Page 20

Generate and Propagate

(35)

S:	—	C _i	—

G		G	

G:	—	A		B	

P		P	

(36)

C _o :	—	C _i	—


G		G	

P:	—	A		B	

P		P	


How Computers Work Lecture 4 Page 21

Implementation of C_o

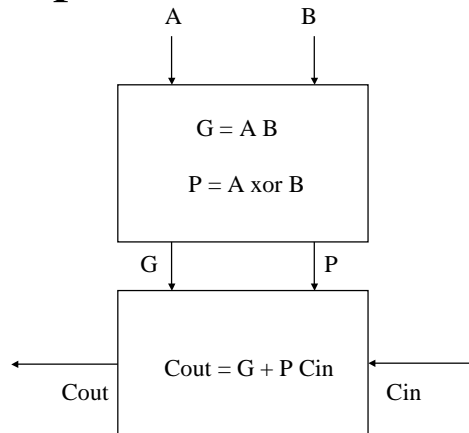

How Computers Work Lecture 4 Page 22


Implementation of S

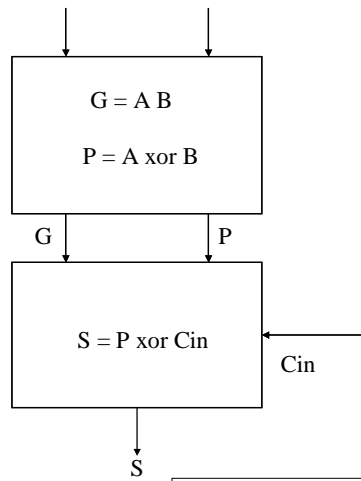

How Computers Work Lecture 4 Page 23


Yet Another Idea !

- Carry Look-Ahead

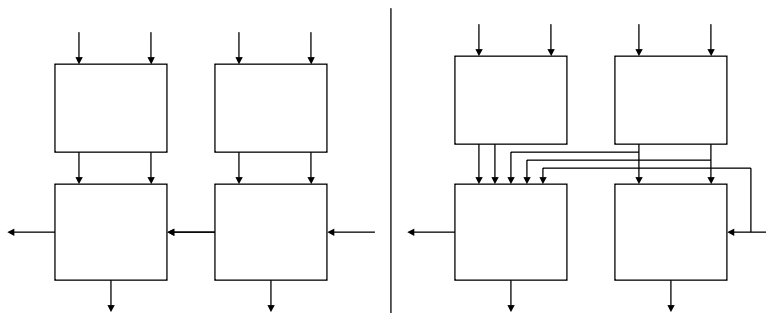

How Computers Work Lecture 4 Page 24

The 74181 ALU

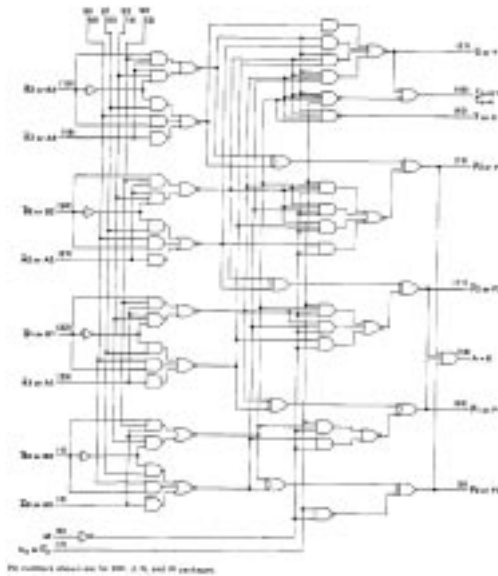

How Computers Work Lecture 4 Page 25

How Fast Can an Adder Get ?

- **Input Sensitivity Analysis:** Ultimately, some bits of the answer are dependent on all bits of the inputs.
- Given an infinite number of **bounded fan-in** gates, what is the minimum growth of t_{pd} vs. the number of inputs (n)?
 - Answer: $O(\log(n))$

How Computers Work Lecture 4 Page 26

Any more tricks to go faster?

- What about changing the Encoding of the inputs (i.e. base 4 !!!!!!!)
 - $O(\log(n))$ limitation still there, but converting to a higher radix, doing the computation, then going back to binary CAN be faster than doing it naively in binary.
- How about analog computing?
 - Works, but watch out for noise.
- How about parallel computing?
 - Works, but watch out for cost.
- How about pipelined computing?
 - Q: What's a pipelined computer?
 - A: You're going to find out real soon.

How Computers Work Lecture 4 Page 27

Summary

- Today's Lecture:
 - How to build the Arithmetic/Logical Unit
 - Time/Space/Cost Trade-offs
- Recitation
 - K-maps and sum-of-products form
 - Multipliers

How Computers Work Lecture 4 Page 28